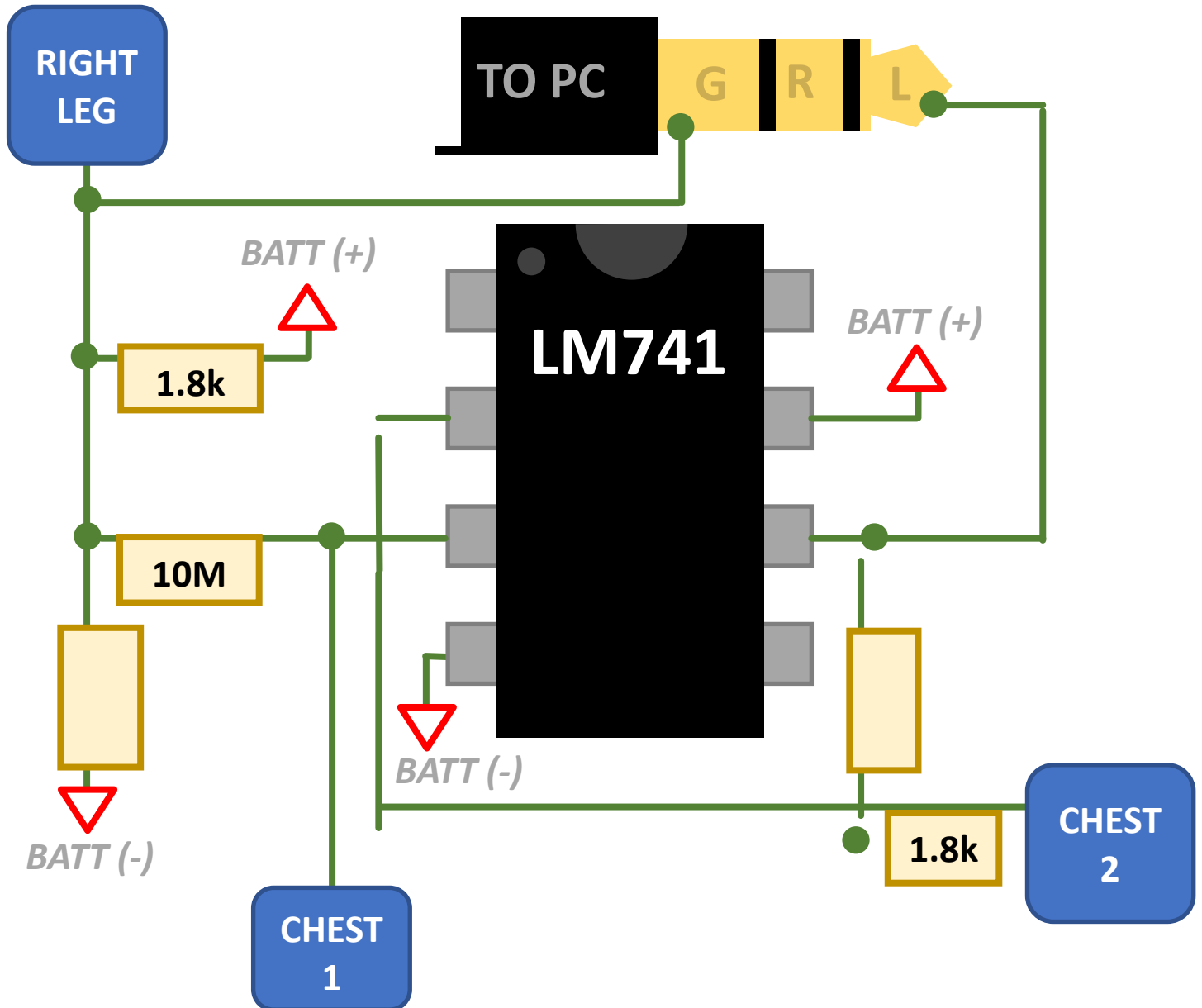


# DIY ECG - SINGLE OP-AMP VERSION

## Hardware -1

### Circuit Diagram



Output is rich in 60Hz noise, but when sharply low-pass filtered to around 45Hz the ECG becomes very clear.